Analysis of Thyristor Based HVDC Transmission SYS

Mr. Manthan Panchal[1]
[1]RMS Polytechnic

Abstract — A high-voltage, direct current (HVDC) electric power transmission system uses direct current for the bulk transmission of electrical power, in contrast with the more common alternating current systems. For long-distance transmission, HVDC systems may be less expensive and suffer lower electrical losses. Originally developed in the 1930s, HVDC technology is only really suited to long-range transmission. This is because of the static inverters that must be used to convert the energy to DC for transmission. These are expensive devices, both in terms of capital cost and energy losses. With contemporary HVDC technology, energy losses can be kept to about 3% per 1000km.. This could be different national grids running on different frequencies; it could be different grids on the same frequency with different timing; finally, it could be the multiple unsynchronized AC currents produced by something like a field of wind turbines.

I. INTRODUCTION

The High Voltage Direct Current Transmission are used for transfer of electric power over a long distance in remote places. The HVDC link are considered better over the HVAC links because of the several reasons discussed below. High-voltage AC transmission links have disadvantages, which may compel a change to DC technology:

1) Inductive and capacitive elements of overhead lines and cables put limits to the transmission capacity and the transmission distance of AC transmission links.
2) This limitation is of particular significance for cables. Depending on the required transmission capacity, the system frequency and the loss evaluation, the achievable transmission distance for an AC cable will be in the range of 40 to 100 km. It will mainly be limited by the charging current.
3) Direct connection between two AC systems with different frequencies is not possible.
4) Direct connection between two AC systems with the same frequency or a new connection within a meshed grid may be impossible because of system instability, too high short-circuit levels or undesirable power flow scenarios.

Therefore the development of a technology for DC transmissions as a supplement to the AC transmission was taken into consideration by the researchers and engineers.

Initially, the mercury valves were used to make line-commuted current sourced convertors for the HVDC links. Then with development of thyristor, better control over the links was possible. Then comes the thyristors with higher current and voltage ratings eliminated the need of the parallel and series connections and hence reduced the size

and improves the control of the convertors.

The advantages of a DC link over an AC link are:

1) A DC link allows power transmission between AC networks with different frequencies or networks, which cannot be synchronized, for other reasons.
2) Inductive and capacitive parameters do not limit the transmission capacity or the maximum length of a DC overhead line or cable. The conductor cross section is fully utilized because there is no skin effect.

For a long cable connection, e.g. beyond 40 km, HVDC will in most cases offer the only technical solution because of the high charging current of an AC cable. This is of particular interest for transmission across open sea or into large cities where a DC cable may provide the only possible solution.

1) A digital control system provides accurate and fast control of the active power flow.
2) Fast modulation of DC transmission power can beused to damp power oscillations in an AC grid and thus improve the system stability.

Considering economic and environmental factors, the HVDC still stand above the HVAC link.

The cost of HVDC and HVAC are calculated over the following factors for a link for 100km;

- AC vs. DC station terminal costs
- AC vs. DC line costs
- AC vs. DC capitalised value of losses

The total cost of the HVDC is found to be very less as compared to the HVAC.

In the project we are using mono-polar long distance transmission convertors. For very long distances and in particular for very long sea cable transmissions, a return path with ground/sea electrodes will be the most feasible solution.
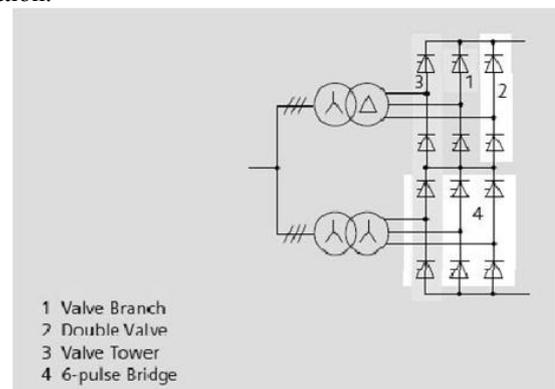

1 Valve Branch
2 Double Valve
3 Valve Tower
4 6-pulse Bridge

Fig. 1

HVDC converters are usually built as 12-pulse circuits. This is a serial connection of two fully controlled 6-pulse converter bridges and requires two 3-phase systems which

are spaced apart from each other by 30 electrical degrees. . The phase difference effected to cancel out the 6-pulse harmonics on the AC and DC side.
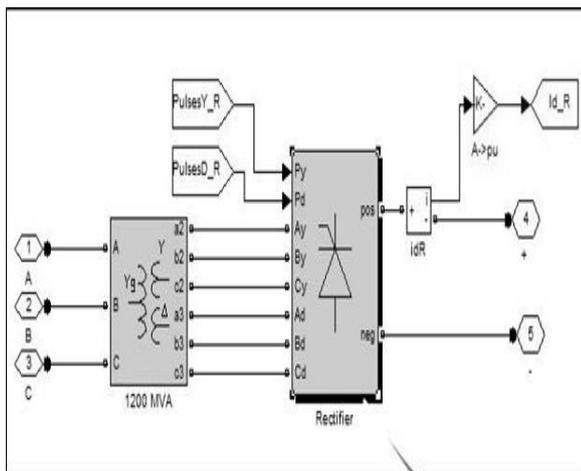

Fig. 2: Arrangement of valve branches in 12-pulse

II.   MAIN COMPONENTS IN HVDC

1) Thyristor valves.
   The thyristor valves make the conversion from AC into DC and thus are the central component of any HVDC converter station. The thyristor valves are of the indoor type and air-insulated.
2) Convertor Transformer.
   The converter transformers transform the voltage of the AC busbar to the required entry voltage of the converter. The 12-pulse converter requires two 3-phase systems which are spaced apart from each other by 30 or50 electrical degrees. This is achieved by installing a transformer on each network side in the vector groups Yy0 and Yd5. At the same time, they ensure the voltage insulation necessary in order to make it possible to connect converter bridges in series on the DC side, as is necessary for HVDC technology.
3) Functions of the Smoothing Reactor
   - Prevention of intermittent current.
   - Limitation of the DC fault currents.
   - Prevention of resonance in the DC circuit.
   - Reducing harmonic currents including.Limitation of telephone interference.
4) Harmonic filters.
The filter arrangements on the AC side of an HVDC converter station have two main duties:
- to absorb harmonic currents generated by the HVDC converter and thus to reduce the impact of the harmonics on the connected AC systems, like AC voltage distortion and telephone interference
- to supply reactive power for compensating the demand of the converter station.
5) Surge Arrestors.
The main task of an arrester is to protect the equipment from the effects of over voltages. During normal operation, it should have no negative effect on the power system. Moreover, the arrester must be able to withstand typical surges without incurring any damage.
6) DC Transmission line.
7) Control and Protection.

Main objectives for the implementation of the HVDC control system are reliable energy transmission which operates highly efficient and flexible energy flow that responds to sudden changes in demand thus contributing to network stability.

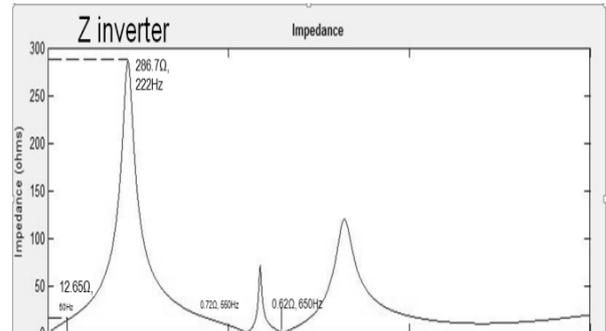## III.   DESCRIPTION OF HVDC TRANSMISSION SYSTEM

Fig. 3

The section illustrates modelling of a high-voltage direct current (HVDC) transmission link using 12-pulse thyristor converters. Perturbations are applied to examine the system performance.

A 1000 MW (500 kV, 2 kA) DC interconnection is used to transmit power from a 500 kV, 5000 MVA, 60 Hz system to a 345 kV, 10000 MVA, 50 Hz system. The AC systems are represented by damped L-R equivalents with an angle of 80 degrees at fundamental frequency (60 Hz or 50 Hz) and at the third harmonic.

The rectifier and the inverter are 12-pulse converters using two Universal Bridge blocks connected in series. The converters are interconnected through a 300-km line and 0.5 H smoothing reactors.

The converter transformers (Wye grounded/Wye/Delta) are modelled with Three-Phase Transformer (Three-Windings) blocks. From the AC point of view, an HVDC converter acts as a source of harmonic currents. From the DC point of view, it is a source of harmonic voltages.
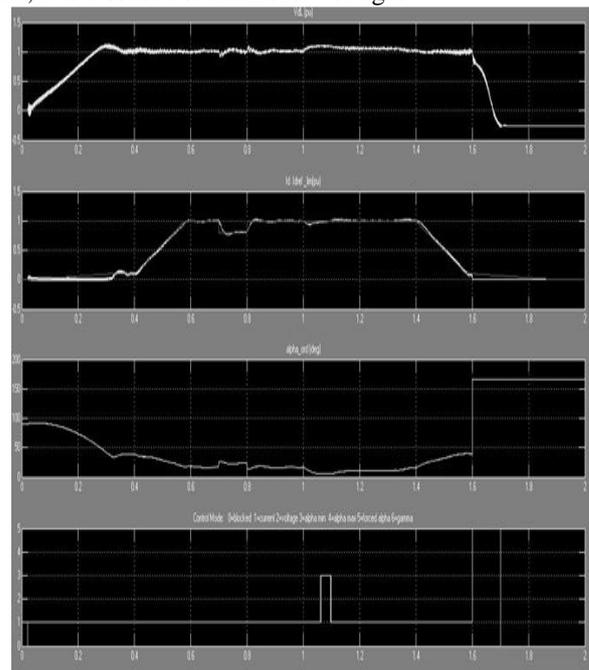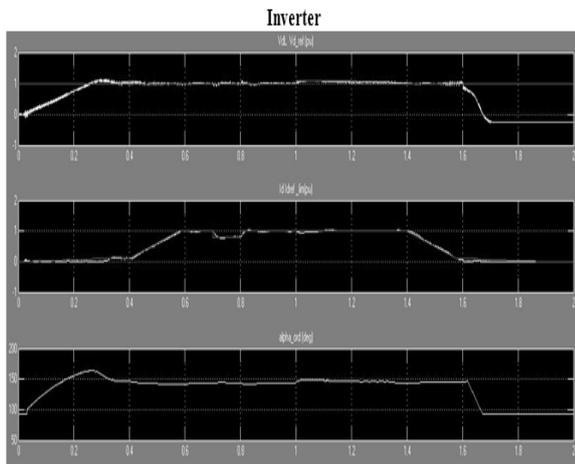

Fig. 4

Inverter

Fig. 5

The order n of these characteristic harmonics is related to the pulse number p of the converter configuration: $n = kp \pm 1$ for the AC current and $n = kp$ for the direct voltage, k being any integer. In the example, $p = 12$, so that injected harmonics on the AC side are 11, 13, 23, 25, and on the DC side are 12, 24.

AC filters are used to prevent the odd harmonic currents from spreading out on the AC system. The filters are grouped in two subsystems. These filters also appear as large capacitors at fundamental frequency, thus providing reactive power compensation for the rectifier consumption due to the firing angle α. For α = 30 degrees, the converter reactive power demand is approximately 60% of the power transmitted at full load. Inside the AC filters subsystem, the high Q (100) tuned filters at the 11th and 13th harmonics and the low Q (3), or damped filter, used to eliminate the higher order harmonics, e.g., 24th and up. Extra reactive power is also provided by capacitor banks.

IV. REFERENCE

[1] Arrilaga, J., High Voltag e Direct Current Transmission, IEEE® Powe r Engineering Series 6, Peter Peregrinu s, Ltd., 1983.

[2] Lidong Zhang, Lars Dofnas, "A Novel Method to Mitigate Commutati on Failures in HVDC Systems," Proc eedings PowerCon 2002. International Co nference on, http://www.mathworks.in/help/toolbox/physmod /powersys/ug/f8-8739.html

[3] Siemens' "High Voltage Direct Current Transmission", http://www.siemens.com/energy/hvdc